



[Course](#) > [Week 9](#) > [Lab 4 : ...](#) > Lab Tas...



Lab Task 4

Doc/Pdf File Submission

After you are done submitting the following lab questions, submit the doc/pdf file and proteus project file [here](#)

The filename must be like this: **Lab_4_StudentID_FullNameWithoutSpace.pdf/doc**. For example, if you are a student whose StudentID is "18101485" and name is "Sowmitra Das", your filename will be: Lab_4_18101485_SowmitraDas.pdf/doc.

Lab Task 4

0 points possible (ungraded)

Use $2N2222$ BJT to find the collector current i_c when

1. base current $i_b = 6\mu A$ and collector emitter voltage $v_{ce} = 0.11 V$
2. base current $i_b = 15\mu A$ and collector emitter voltage $v_{ce} = 0.71 V$
3. base current $i_b = 14\mu A$ and collector emitter voltage $v_{ce} = 0.66 V$
4. base current $i_b = 7\mu A$ and collector emitter voltage $v_{ce} = 0.95 V$
5. base current $i_b = 14\mu A$ and collector emitter voltage $v_{ce} = 0.28 V$

Create a table with the above 5 values of collector current i_c along with corresponding base current i_b and collector emitter volage v_{ce} and submit it in the google form . You don't need to write anything else

Submit

i Answers are displayed within the problem

◀ Previous

Next ▶

© All Rights Reserved

[About Us](#)

[BracU Home](#)

[USIS](#)

[Course Catalog](#)

Copyright - 2020