

Course > Week 4 > Lab 1 - ... > Lab Tas... < 用 >

## Lab Task 1

## Simulation File Submission

After you are done submitting the following lab questions, submit the simulation-file of your circuit with the ".pdsprj" extension (this will be in the folder where you saved your project) here.

The filename must be like this:

Lab 1 StudentID FullNameWithoutSpace.pdsprj. For example, if you are a student whose StudentID is "18101485" and name is "Sowmitra Das", your filename will be: Lab\_1\_18101485\_SowmitraDas.pdsprj.

## **IV - Characteristics**

4/4 points (graded)

Plot the IV-Characteristics of the diode model S5AC in PROTEUS.

Perform a DC Sweep Analysis and plot the graph from 0 Volt to 0.8 Volt. Use 10, 000 steps between the Start Value and Stop Value. From the graph, answer the following questions -

1. If the forward voltage across the diode is 0.65 Volt, what is the current through the diode? [Answer in mA. Input at least 3 digits after the decimal point.]

<sup>21</sup> I 5.99	Lab Task 1   Lab 1 - Diode IV Cha	racteristics   CSE251 Courseware	buX   BRAC Univer
3.33			

2. If the forward voltage across the diode is 0.72 Volt, what is the current through the diode? [Answer in mA. Input at least 3 digits after the decimal point.]

29.60		mA	<b>~</b>	•
-------	--	----	----------	---


3. If the current through the diode is 6.8 mA, what is the forward voltage across the diode? [Answer in Volt. Input at least 3 digits after the decimal point.]



4. If the current through the diode is 15.1 mA, what is the forward voltage across the diode? [Answer in Volt. Input at least 3 digits after the decimal point.]



Submit You have used 6 of 7 attempts

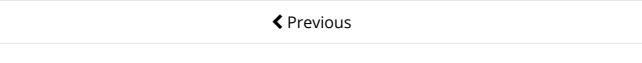



© All Rights Reserved

About Us

**BracU Home** 

USIS

Course Catalog

Copyright - 2020